

Challenges of Magnetic Component Core and Copper Loss Measurement

Weyman Lundquist, Engineering Manager

Mary E. Clark, Research and Development Engineer

03/20/2019

Isolation of core and winding loss in a transformer or inductor can prove a challenging task.


Device must be evaluated prior to test to establish if extraction is useful

Simulation might be more accurate and faster choice

Results must be interpreted carefully

Measurement error can provide incorrect results that may or may not be easily caught

Goals using an impedance analyzer

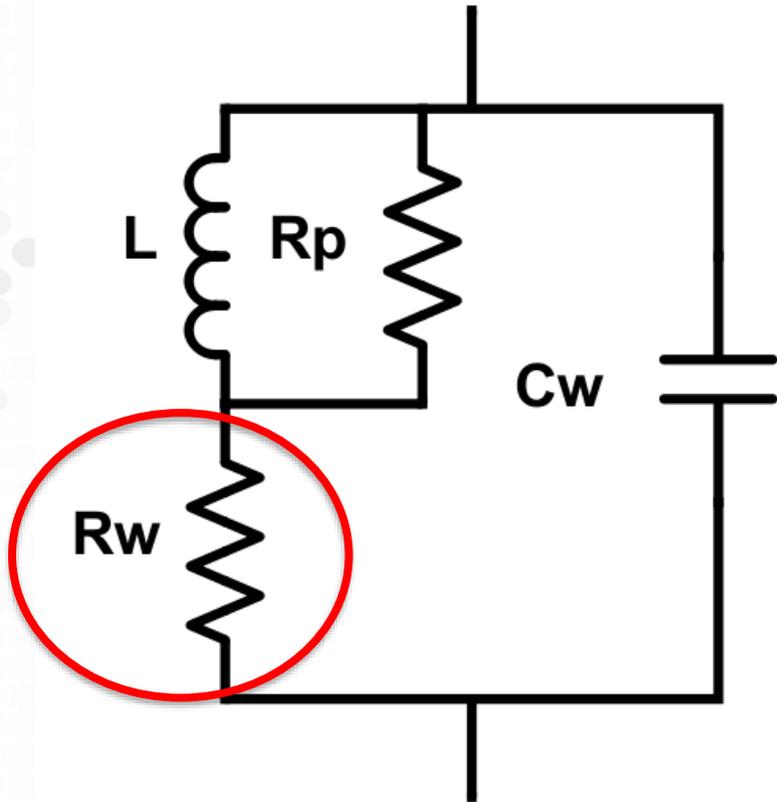

Model magnetic device per the schematic at left.

From impedance analyzer gain 2 measurements – R_m , X_m .(real and imaginary impedance, can be extracted from Z and phase angle)

Require two more measurements to solve system and extract R_w .

Need to find C_w and R_p .

Find Cw using DUT's self-resonant frequency


$$\text{Use } C = \frac{1}{L(2\pi f)^2}$$

$$\text{In this example, } C = \frac{1}{7 * 10^{-6} (2 * \pi * 13.8 * 10^6)^2} = 19 \text{ pF}$$


Limitations:

C can vary with frequency

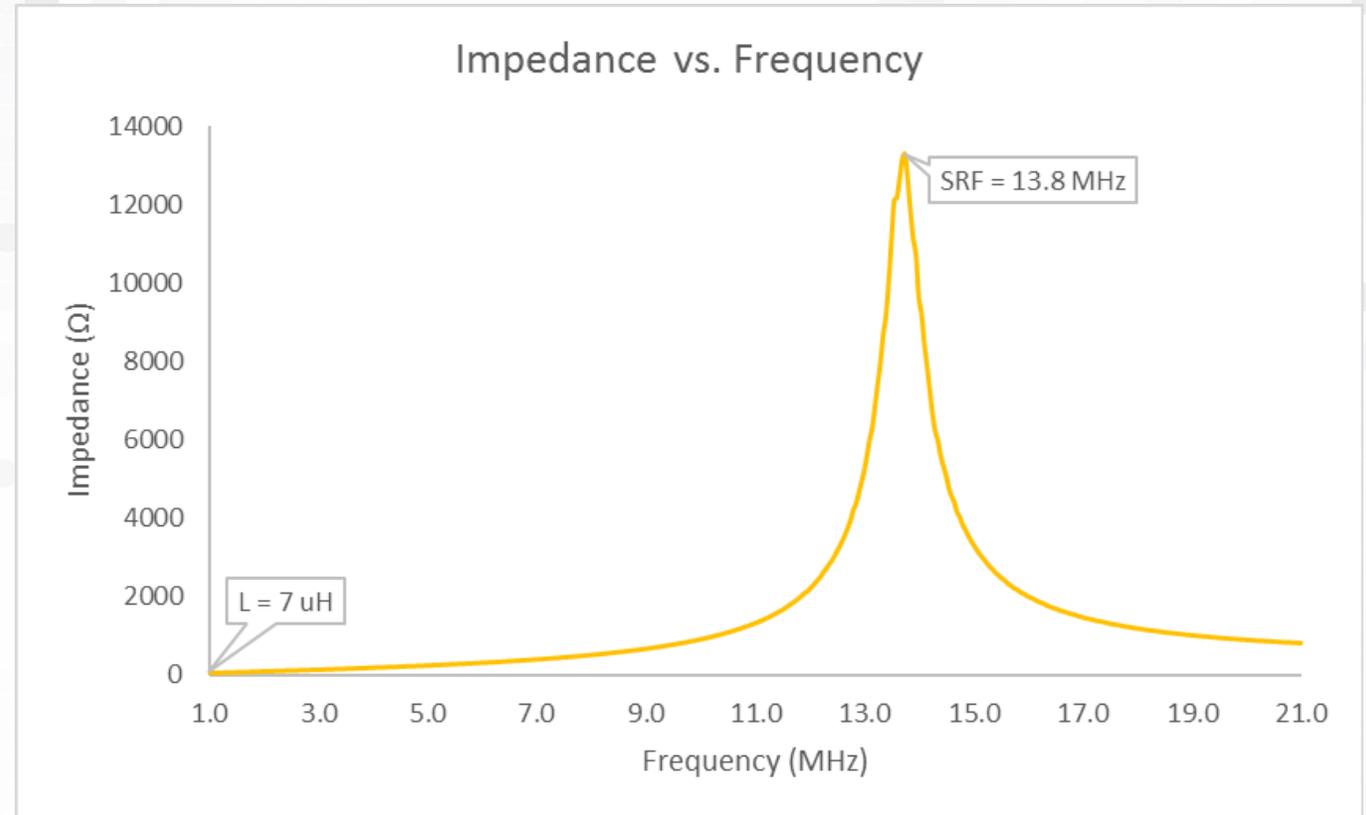L can vary with frequency (we measure L at low frequency)



Find R_p with 2 winding measurement

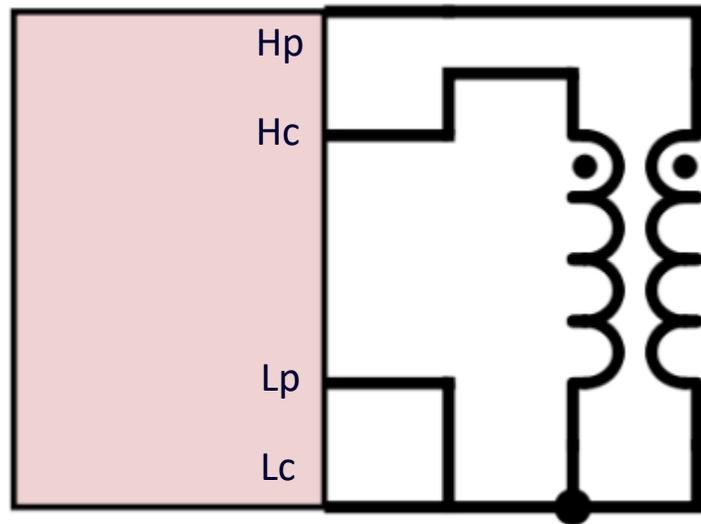

R_p test device construction:

Construct 1:1 transformer with same # of turns as winding of interest.

Use fine wire and no gap to reduce Q of the test transformer.

Keep windings as far apart from each other as possible to minimize mutual resistance, interwinding capacitance.

Test method:

Set test frequency to frequency of interest

Utilize 4 port LCR meter/impedance analyzer such as HP4285A

Connect DUT per schematic

Measure R_p through L_p - R_p mode

Alternate method: use manufacturer's datasheet to obtain R_p

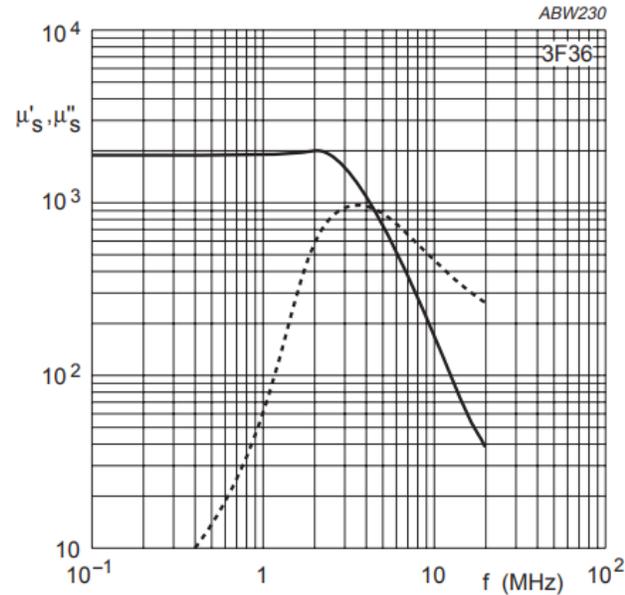


Fig.1 Complex permeability as a function of frequency.

For an ungapped core, impedance is $Z_{ungapped} = \frac{j \omega N^2}{A_e \mu^* \mu_0}$

μ^* is complex permeability (function of frequency)

l_e is the path length

A_e is the core area

μ_0 is the permeability of free space

N is the number of turns

ω is the frequency

$$R_p = \frac{1}{\text{Real}\left[\frac{1}{Z_{ungapped}}\right]}$$

Can obtain all parameters from datasheet and build to obtain R_p as a function of frequency.

With C_w and R_p , can solve for R_w

Full method:

Define Z_{magnetic} of L , R_p :

$$\frac{1}{j\omega L} + \frac{1}{R_p} = \frac{1}{Z_{\text{magnetic}}}$$

Solve for R_w in the network


$$\frac{1}{R_w + Z_{\text{magnetic}}} + \frac{1}{\frac{-j}{\omega C}} = \frac{1}{R_m + jX_m}$$

$$R_w = \text{Real} \left[\frac{1}{\frac{1}{R_m + jX_m} + \frac{1}{\frac{j}{\omega C}}} - Z_{\text{magnetic}} \right]$$

Limitations:

C can vary with frequency

L can vary with frequency

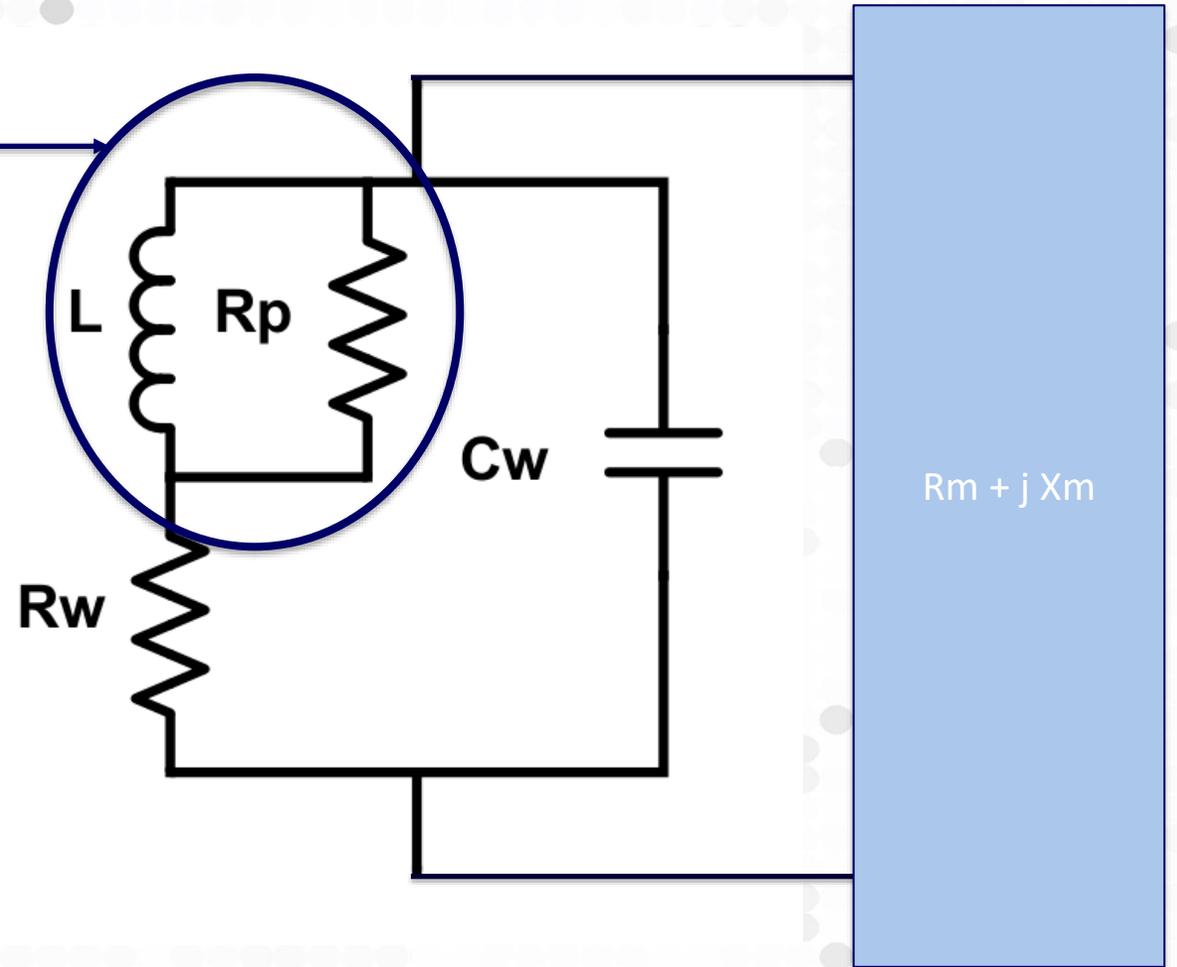

With Cw and Rp, can solve for Rw


Simple method

Subtract off capacitance and Rp effect in parallel space

$$\frac{1}{R_w + j X_{inductor}} = \frac{1}{R_m + j X_m} - j \omega C - \frac{1}{R_p}$$

$$R_w = \text{Real}\left[\frac{1}{\frac{1}{R_m + j X_m} - j \omega C - \frac{1}{R_p}}\right]$$

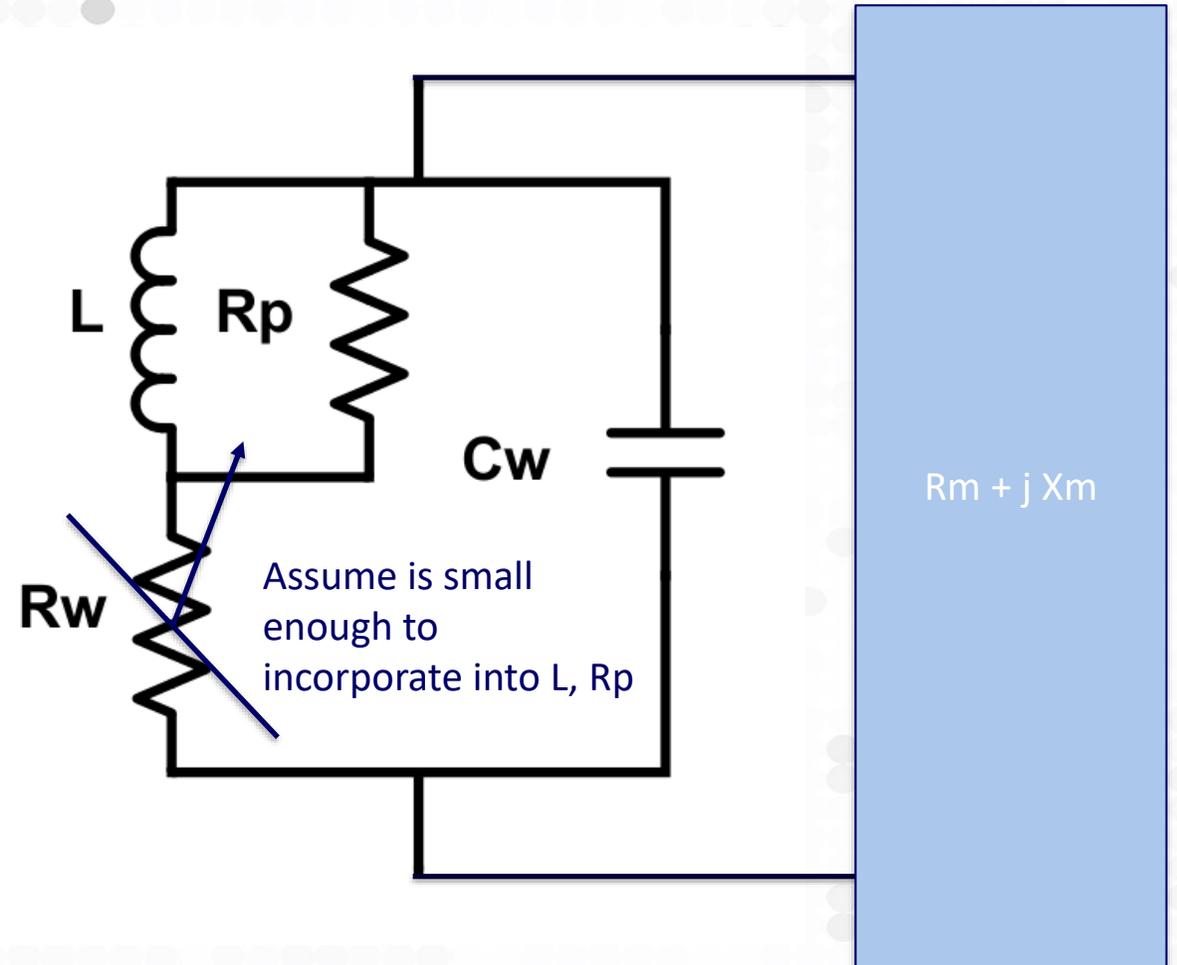****This expression is only valid when Rw is small compared to the real part of L, Rp parallel combination****




Example

15 turn inductor on Fair-Rite 5943002701 core, measure from 100 kHz to 500 kHz in 25 kHz steps.


Calculate R_p from manufacturer's data:

Electrical Properties	
A_L (nH)	885 ±20%
A_e (cm ²)	0.79
$\Sigma l/A$ (cm ⁻¹)	11.2
l_e (cm)	8.9
V_e (cm ³)	7

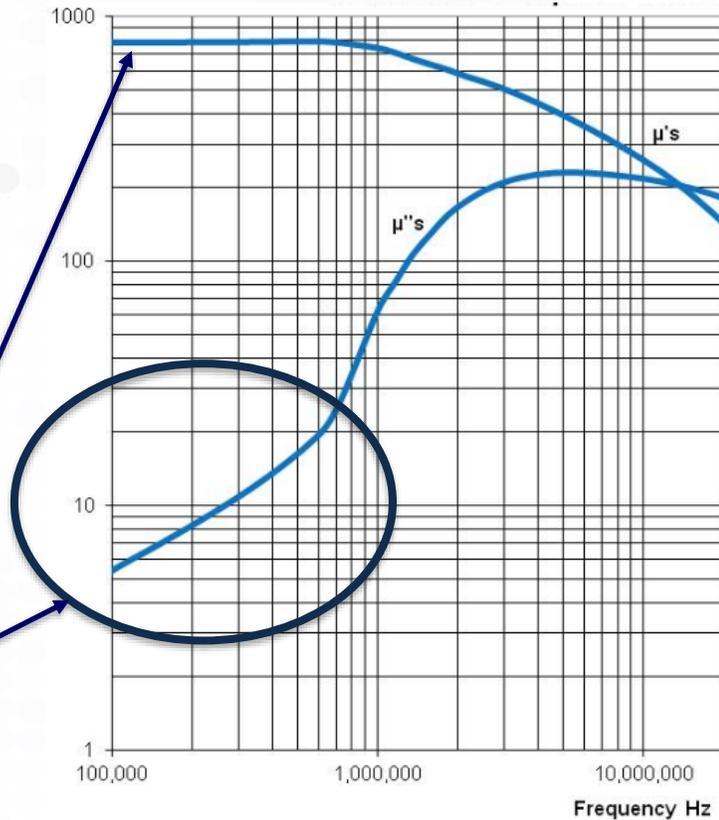

μ' is constant in the range of interest

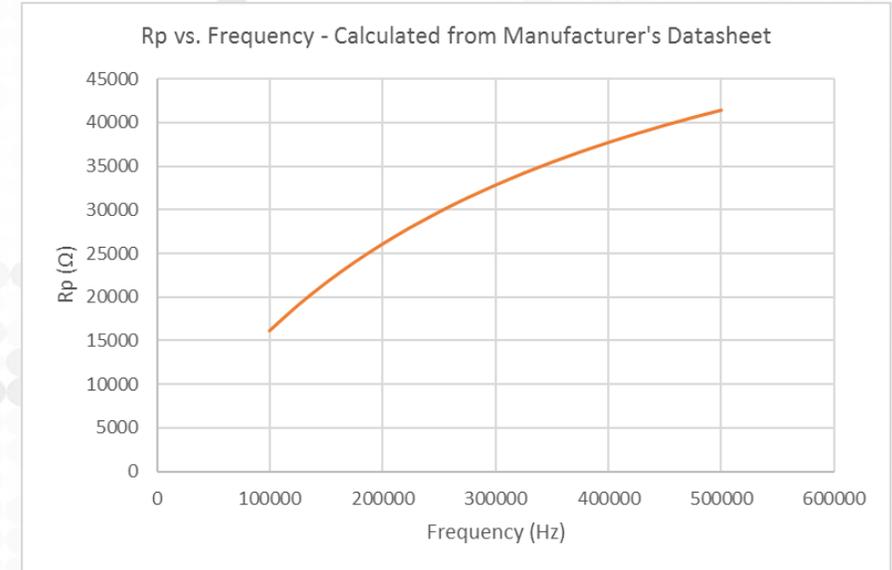
μ'' is linear – create line to fit beginning and end point



R_p increases with frequency

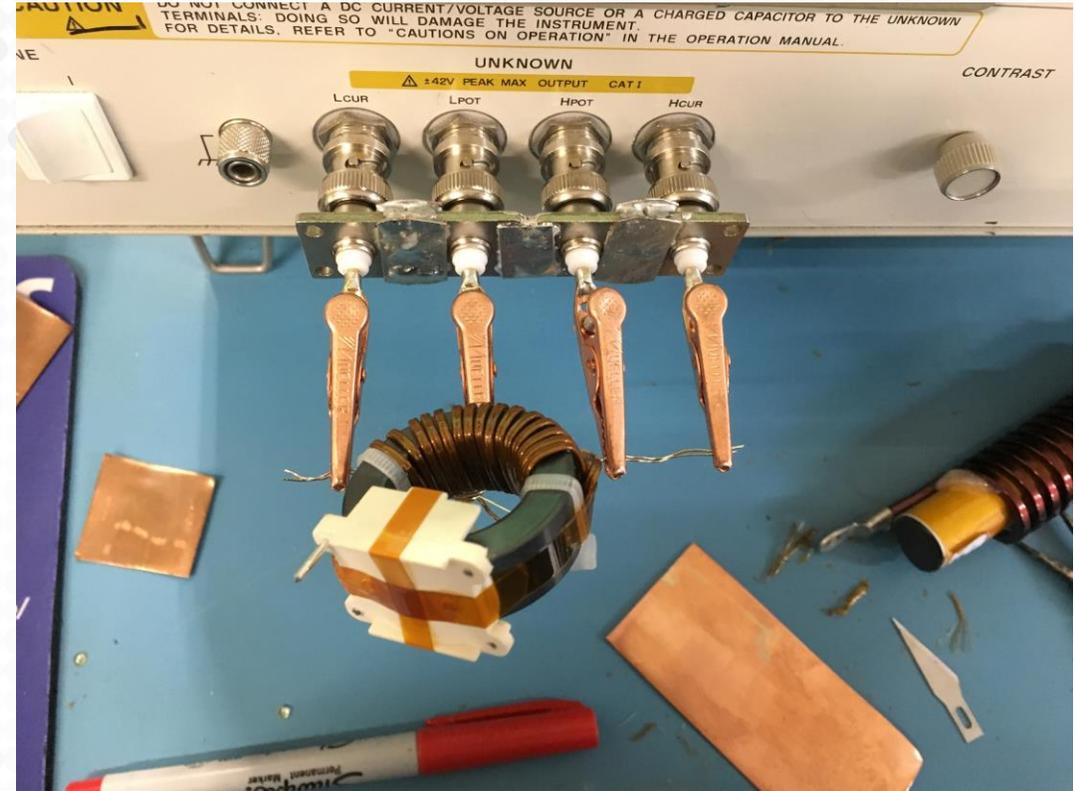Example

Measure R_m and X_m on impedance analyzer - used HP4285A in example.



Use short fixture, with current injection and voltage measurement clips separate, to minimize stray resistance and inductance


Example

Measure R_m , X_m , SRF on impedance analyzer. Use SRF, low frequency inductance, to calculate capacitance.

Plug values to formula and extract R_w .


$$R_w = \text{Real} \left[\frac{1}{\frac{1}{R_m + j X_m} + \frac{1}{\frac{j}{\omega C_w}}} - Z_{\text{magnetic}} \right]$$

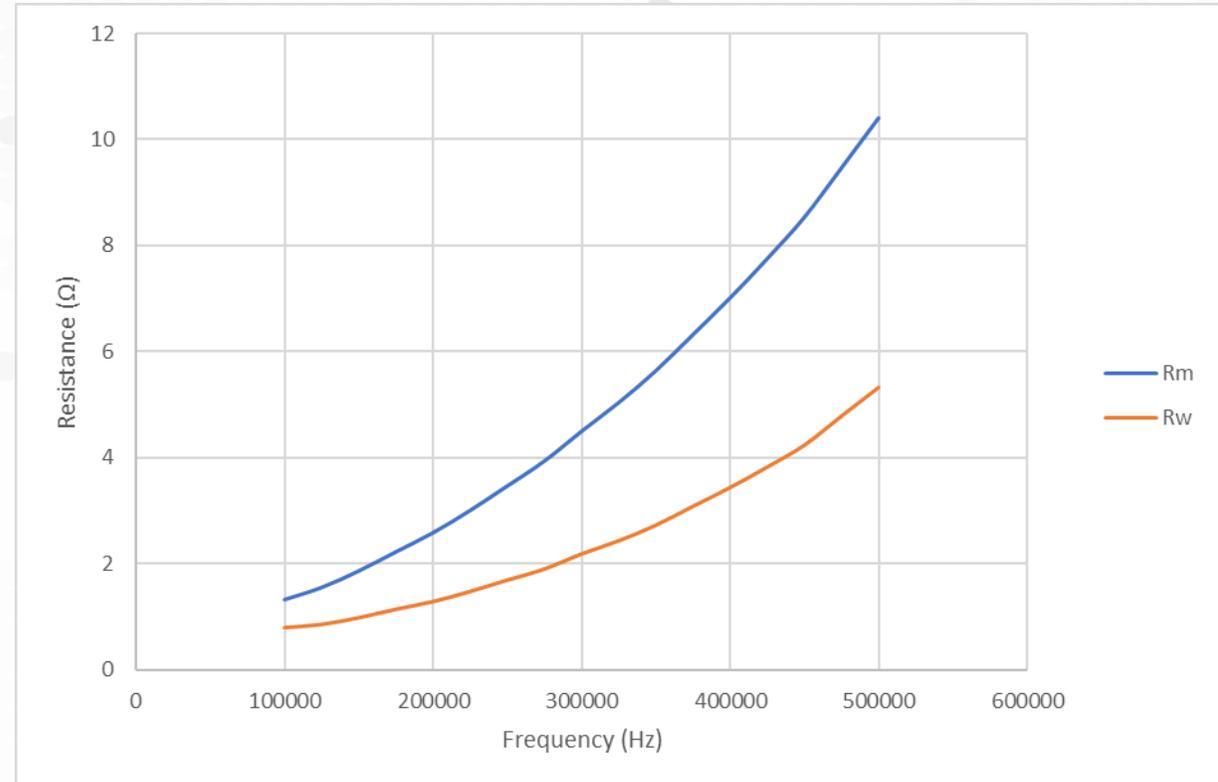Physical result – R_w increases with frequency




Errors

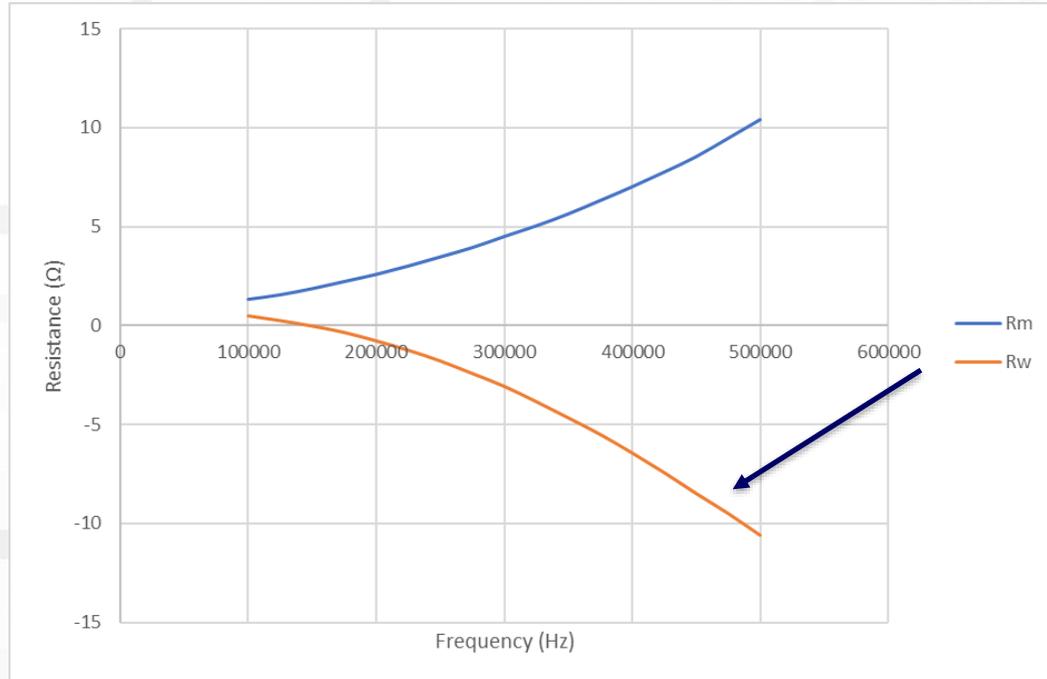Obvious error:
extracted resistance is negative



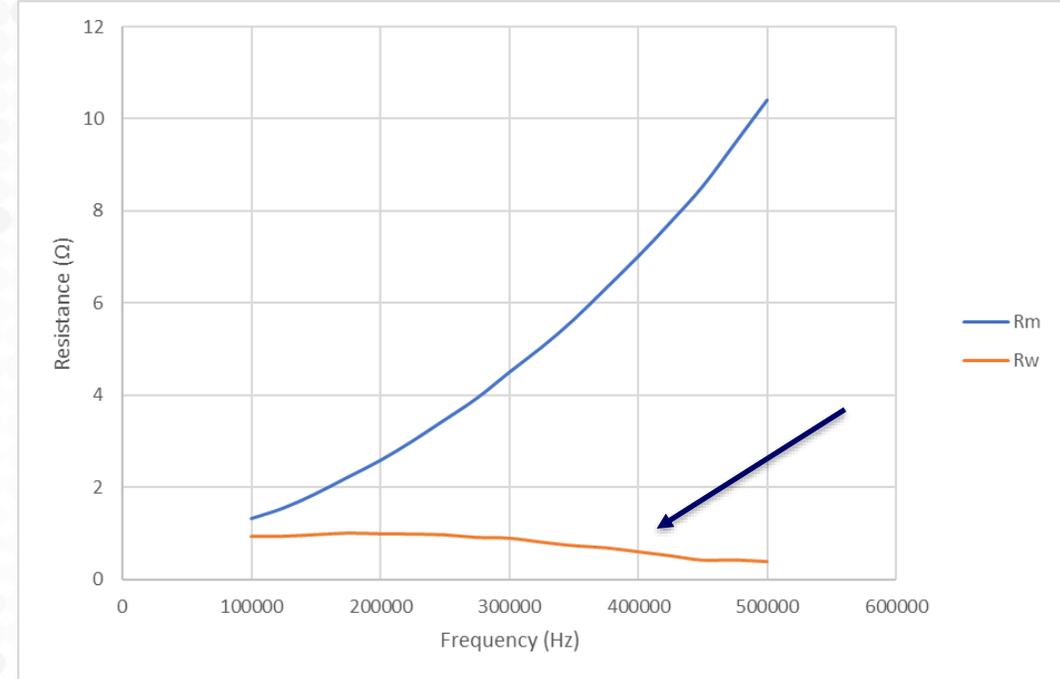Less obvious error:
extracted resistance trends
downward – not a physical result



REFERENCE

“A Step-by-Step Guide to Extracting Winding Resistance from an Impedance Measurement”

Benedict X. Foo, Aaron L.F. Stein, Charles R. Sullivan

Presented at APEC 2016